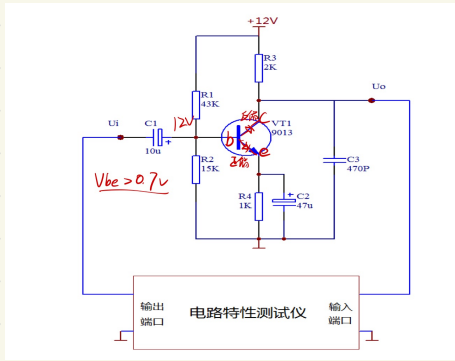




$$R_i = R_1 // R_2 // [r_{be} + (1 + \beta) R_e]$$

$$= 43k // 15k //$$

$$= 11.12k //$$

$$\approx 11.12k$$

$$R_o \approx R_3 \approx 2k\Omega$$

Normal: $\approx 5.08k\Omega$
 $V_o = 4.80V$ $V_o = 1.44V$

$$4.8V \quad 5.1k\Omega \quad 1.44V$$

$$5.1k: 4.8 - 1.44$$

$$\frac{R_i}{1.44} = \frac{5.1k}{4.8 - 1.44}$$

$$R_i = 2185.7k\Omega$$

$$4.40V \quad 1.44V$$

$$2.96$$

$$4.4V \quad 1.44$$

$$5.11k \quad 30m \quad 12m \quad R_i$$

$$5.11 \times \frac{12}{18} = 3.4P\Omega$$

$$V_o = 1.34V$$

$$4.4V$$